

Connections:-

Image 1:-

Connections to bolt module:

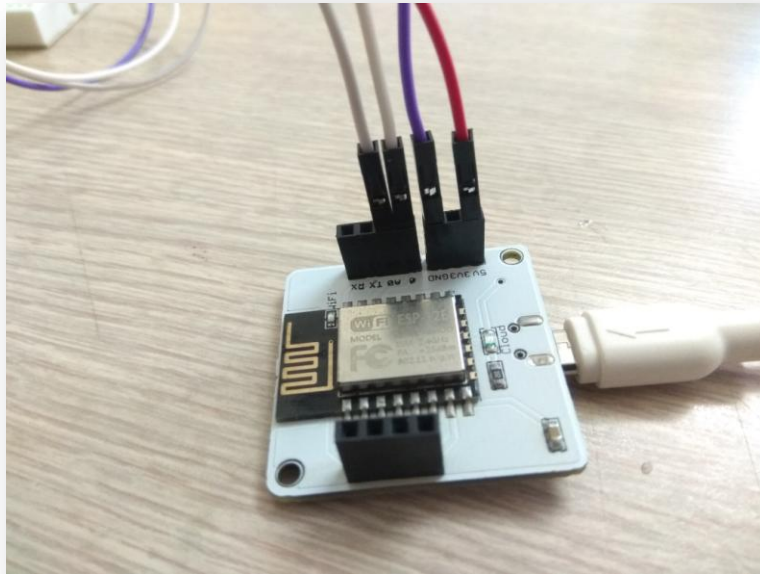


Image 2:

Connecting breadboard and led

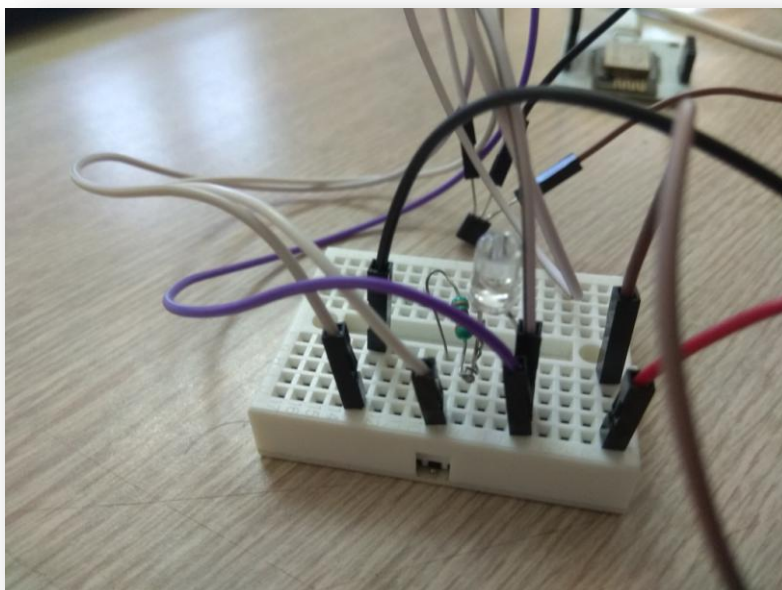


Image 3:

Connecting LM35 by female to male jumper wire

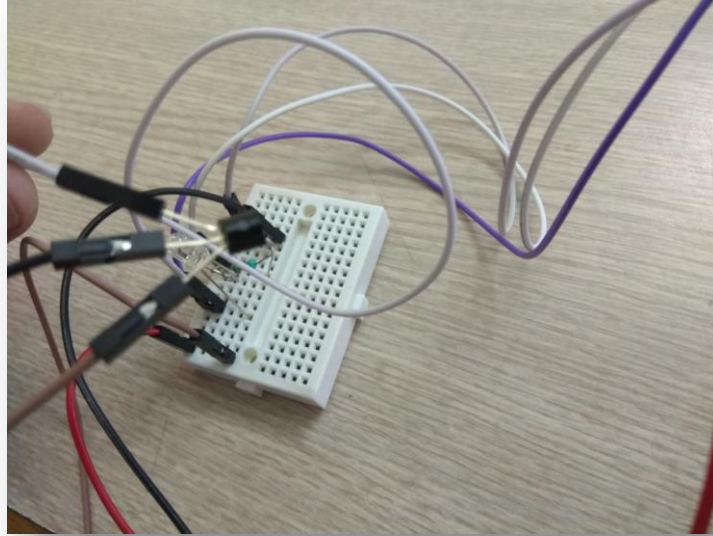


Image 4:

Circuit after giving power supply

